



EEC2146: Electronic Circuits and Measurements

Prepared by:
Dr. Hossam Kasem

Email:
hossam.kasem@f-eng.tanta.eg
hossamkasem1@gmail.com



EEC2146: Electronic Circuits and Measurements

LEC: 2 Review On FET Transistor



EEC2146: Electronic Circuits and Measurements



FET Transistors

Objectives and outline:

1. Structure of FET transistors
2. Basic operation
3. Modes of operation
5. I-V characteristics of A practical FET
6. DC analysis
7. Small signal model of FET
8. AC analysis of FET Amplifiers



FET Transistors

Comparison between BJT and FET


Similarities: Amplifiers.
Switching devices.
Impedance matching circuits.

Differences: FETs are voltage controlled devices. BJTs are current controlled devices.
FETs have higher input impedance. BJTs have higher gain.
FETs are less sensitive to temperature variations and are better suited for integrated circuits
FETs are generally more static sensitive than BJTs.



FET Transistors

Types of FET

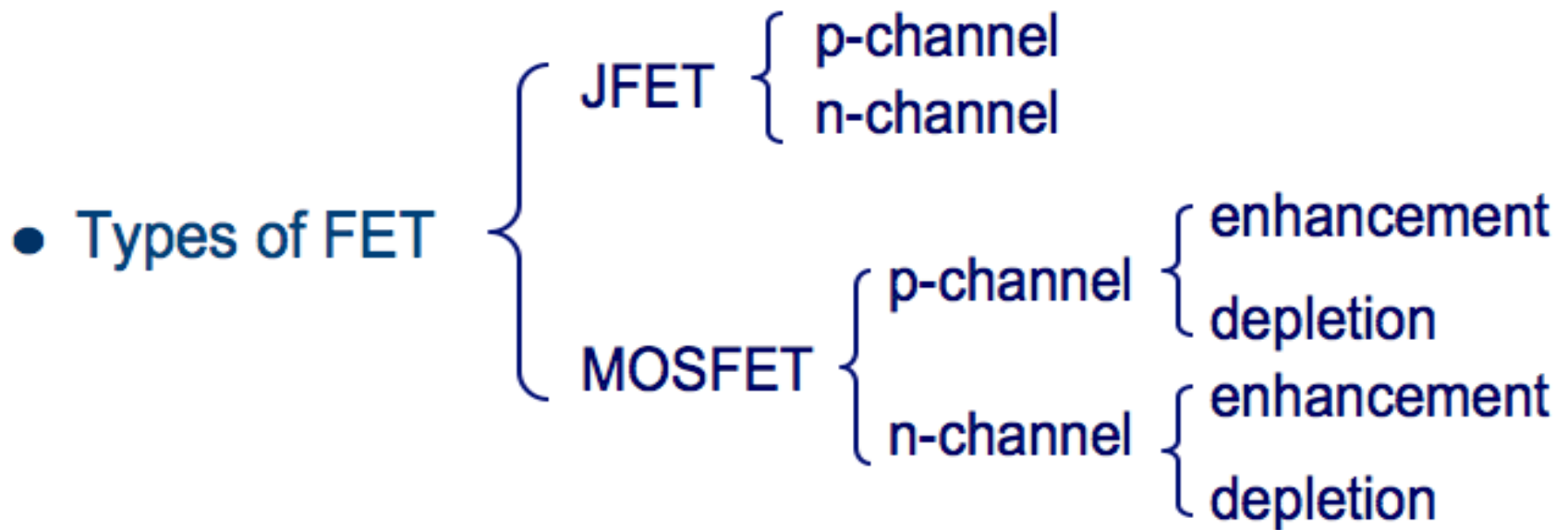



FET Transistors

JFET (N-Channel)

There are two types of JFETs:


n-channel

p-channel

JFETs have three terminals:

The **Drain** (D) and **Source** (S) are connected to the *n*-channel

 The **Gate** (G) is connected to the *p*-type material






FET Transistors

JFET (N-Channel)

The **source** is the accumulation of electrons at the negative pole of the drain-source voltage.

The **drain** is the electron deficiency (or holes) at the positive pole of the applied voltage.

The **gate** controls the width of the n-channel and, therefore, the flow of charges from source to drain.

 




EEC2146: Electronic Circuits and Measurements

FET Transistors

JFET (N-Channel)
 
$$I_D = I_{DSS} \left(1 - \frac{V_{GS}}{V_P} \right)^2$$



Dr.Hossam kasem

Electronics and Electrical Comm. Dept.




EEC2146: Electronic Circuits and Measurements

FET Transistors

JFET (N-Channel)
 
$$I_D = I_{DSS} \left(1 - \frac{V_{GS}}{V_P} \right)^2$$



Dr.Hossam kasem

Electronics and Electrical Comm. Dept.



EEC2146: Electronic Circuits and Measurements

FET Transistors

Important Relations


<i>JFET</i>		<i>BJT</i>
$I_D = I_{DSS} \left(1 - \frac{V_{GS}}{V_P} \right)^2$	\Leftrightarrow	$I_C = \beta I_B$
$I_D = I_S$	\Leftrightarrow	$I_C \cong I_E$
$I_G \cong 0 \text{ A}$	\Leftrightarrow	$V_{BE} \cong 0.7 \text{ V}$




EEC2146: Electronic Circuits and Measurements

FET Transistors

JFET Symbols

 

N-Channel

 

P-Channel



EEC2146: Electronic Circuits and Measurements



FET Transistors

MOSFET

MOSFETs have characteristics similar to those of JFETs and additional characteristics that make them very useful.

There are two types of MOSFETs:

Depletion-Type


Enhancement-Type



FET Transistors

MOSFET (Depletion type)

The **Drain (D)** and **Source (S)** connect to the n -type regions. These n -typed regions are connected via an n -channel. This n -channel is connected to the **Gate (G)** via a thin insulating layer of silicon dioxide (SiO_2). The n -type material lies on a p -type substrate that may have an additional terminal connection called the **Substrate (SS)**.

 




EEC2146: Electronic Circuits and Measurements

FET Transistors

MOSFET (Depletion type)

 




EEC2146: Electronic Circuits and Measurements



FET Transistors

MOSFET (Depletion type)

 




FET Transistors

MOSFET (Enhancement type)

The **Drain (D)** and **Source (S)** connect to the n -type regions. These n -type regions are connected via an n -channel

 - The **Gate (G)** connects to the p -type substrate via a thin insulating layer of silicon dioxide (SiO_2)
- There is no channel
- The n -type material lies on a p -type substrate that may have an additional terminal connection called the **Substrate (SS)**





FET Transistors

MOSFET (Enhancement type)

The enhancement-type MOSFET (E-MOSFET) operates only in the enhancement mode.


V_{GS} is always positive

As V_{GS} increases, I_D increases

As V_{GS} is kept constant and V_{DS} is increased, then I_D saturates (I_{DSS}) and the saturation level (V_{DSSsat}) is reached

Dr.Hossam kasem

Electronics and Electrical Comm. Dept.

 





EEC2146: Electronic Circuits and Measurements





FET Transistors

MOSFET (Enhancement type)

n-channel

  

p-channel

  



EEC2146: Electronic Circuits and Measurements

FET Transistors

Important Relations

$$I_D = k(V_{GS} - V_T)^2$$

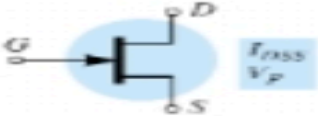
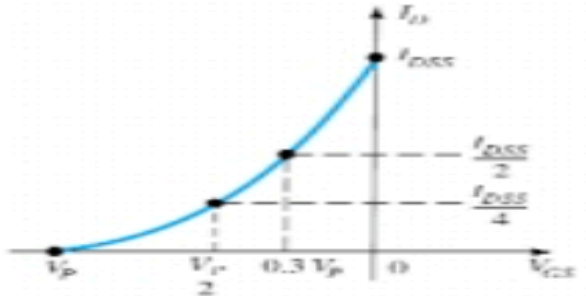
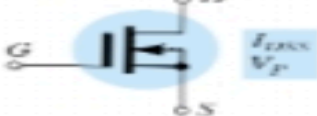
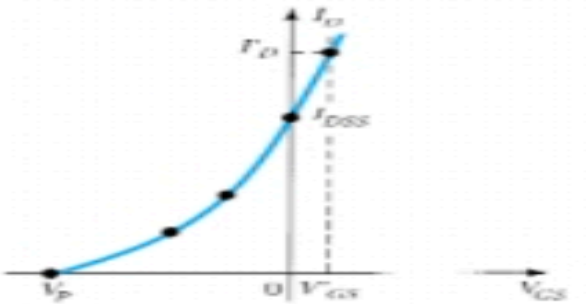
$$k = \frac{I_{D(on)}}{(V_{GS(on)} - V_T)^2}$$



EEC2146: Electronic Circuits and Measurements

FET Transistors

Summary:

Type	-Symbol- Basic Relationships	Transfer Curve
JFET (n-channel)	$I_G = 0 \text{ A}, I_D = I_S$  $I_D = I_{DSS} \left(1 - \frac{V_{GS}}{V_P}\right)^2$	
MOSFET depletion-type (n-channel)	$I_G = 0 \text{ A}, I_D = I_S$  $I_D = I_{DSS} \left(1 - \frac{V_{GS}}{V_P}\right)^2$	




EEC2146: Electronic Circuits and Measurements

FET Transistors


Summary:

MOSFET
enhancement-type
(n-channel)

 

$$I_D = k (V_{GS} - V_{GS(th)})^2$$

$$k = \frac{I_{D(on)}}{(V_{GS(on)} - V_{GS(th)})^2}$$

 



EEC2146: Electronic Circuits and Measurements

FET Transistors

DC Analysis

$$I_G \cong 0 \text{ A}$$

$$I_D = I_S$$

$$I_D = I_{DSS} \left(\frac{1 - V_{GS}}{V_P} \right)^2$$



$$I_D = k(V_{GS} - V_T)^2$$



EEC2146: Electronic Circuits and Measurements

FET Transistors

DC Analysis (Fixed Bias)

  



EEC2146: Electronic Circuits and Measurements

FET Transistors

DC Analysis (Fixed Bias)

 


Figure 6.2

$$-V_{GG} - V_{GS} = 0$$

$$V_{GS} = -V_{GG}$$

$$I_D = I_{DSS} \left(1 - \frac{V_{GS}}{V_P} \right)^2$$

$$+V_{DS} + I_D R_D - V_{DD} = 0$$

$$V_{DS} = V_{DD} - I_D R_D$$



EEC2146: Electronic Circuits and Measurements

FET Transistors

DC Analysis (Fixed Bias)

 


Figure 6.2



$$V_S = 0 \text{ V}$$

$$V_D = V_{DS}$$



$$V_G = V_{GS}$$



EEC2146: Electronic Circuits and Measurements

FET Transistors

DC Analysis (Self Bias)

  

$$V_{GS} = -I_D R_S$$

$$I_D = I_{DSS} \left(1 - \frac{V_{GS}}{V_P} \right)^2$$
$$= I_{DSS} \left(1 - \frac{-I_D R_S}{V_P} \right)^2$$

$$I_D = I_{DSS} \left(1 + \frac{I_D R_S}{V_P} \right)^2$$


$$I_D^2 + K_1 I_D + K_2 = 0$$



EEC2146: Electronic Circuits and Measurements

FET Transistors

DC Analysis (Self Bias)

 

$$V_{DS} = V_{DD} - I_D(R_S + R_D)$$

$$V_S = I_D R_S$$

$$V_G = 0 \text{ V}$$



$$V_D = V_{DS} + V_S = V_{DD} - V_{R_D}$$



EEC2146: Electronic Circuits and Measurements

FET Transistors

DC Analysis (Voltage Divider)

 
 




EEC2146: Electronic Circuits and Measurements

FET Transistors

DC Analysis (Voltage Divider)

  

$$V_G = \frac{R_2 V_{DD}}{R_1 + R_2}$$

$$V_G - V_{GS} - V_{RS} = 0$$
$$V_{GS} = V_G - V_{RS}$$


$$V_{GS} = V_G - I_D R_S$$



EEC2146: Electronic Circuits and Measurements

FET Transistors

DC Analysis (Voltage Divider)

 

$$V_{DS} = V_{DD} - I_D(R_D + R_S)$$

$$V_D = V_{DD} - I_D R_D$$

$$V_S = I_D R_S$$

$$I_{R_1} = I_{R_2} = \frac{V_{DD}}{R_1 + R_2}$$



FET Transistors

DC Analysis (Depletion MOSFET)

The similarities in appearance between the transfer curves of JFETs and depletion- type MOSFETs permit a similar analysis of each in the dc domain. The primary difference between the two is the fact that depletion-type MOSFETs permit operating points with positive values of V_{GS} and levels of I_D that exceed I_{DSS} . In fact, for all the configurations discussed thus far, the analysis is the same if the JFET is replaced by a depletion-type MOSFET.



EEC2146: Electronic Circuits and Measurements

FET Transistors

DC Analysis (Enhancement MOSFET)



$$I_D = k(V_{GS} - V_{GS(Th)})^2$$

$$k = \frac{I_{D(on)}}{(V_{GS(on)} - V_{GS(Th)})^2}$$



FET Transistors

DC Analysis (Enhancement MOSFET)

  




EEC2146: Electronic Circuits and Measurements

FET Transistors

DC Analysis (Enhancement MOSFET)

 

$$V_D = V_G$$

$$V_{DS} = V_{GS}$$

$$V_{DS} = V_{DD} - I_D R_D$$


$$V_{GS} = V_{DD} - I_D R_D$$



EEC2146: Electronic Circuits and Measurements

FET Transistors

DC Analysis (Voltage Divider)

 

$$V_G = \frac{R_2 V_{DD}}{R_1 + R_2}$$

$$+V_G - V_{GS} - V_{R_S} = 0$$

$$V_{GS} = V_G - V_{R_S}$$

$$V_{GS} = V_G - I_D R_S$$

$$V_{R_S} + V_{DS} + V_{R_D} - V_{DD} = 0$$

$$V_{DS} = V_{DD} - V_{R_S} - V_{R_D}$$

$$V_{DS} = V_{DD} - I_D (R_S + R_D)$$



EEC2146: Electronic Circuits and Measurements

FET Transistors

DC Analysis (Summary)

Type	Configuration	Pertinent Equations	Graphical Solution
JFET Fixed-bias		$V_{GSQ} = -V_{GG}$ $V_{DS} = V_{DD} - I_D R_D$	
JFET Self-bias		$V_{GS} = -I_D R_S$ $V_{DS} = V_{DD} - I_D (R_D + R_S)$	
JFET Voltage-divider bias		$V_G = \frac{R_2 V_{DD}}{R_1 + R_2}$ $V_{GS} = V_G - I_D R_S$ $V_{DS} = V_{DD} - I_D (R_D + R_S)$	



EEC2146: Electronic Circuits and Measurements









FET Transistors

DC Analysis (Summary)

JFET Common-gate		$V_{GS} = V_{SS} - I_D R_S$ $V_{DS} = V_{DD} + V_{SS} - I_D (R_D + R_S)$	
JFET ($V_{GSQ} = 0$ V)		$V_{GSQ} = 0$ V $I_{DQ} = I_{DSS}$	
JFET ($R_D = 0$ Ω)		$V_{GS} = -I_D R_S$ $V_D = V_{DD}$ $V_S = I_D R_S$ $V_{DS} = V_{DD} - I_S R_S$	

FET Transistors

DC Analysis (Summary)

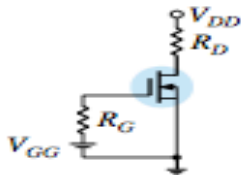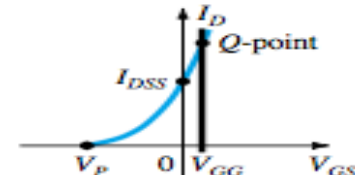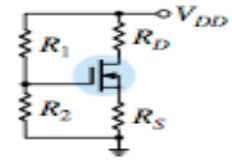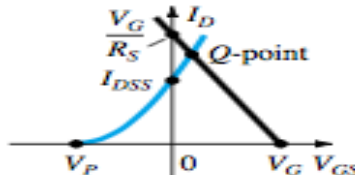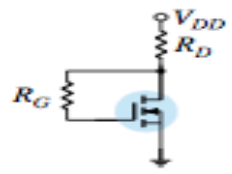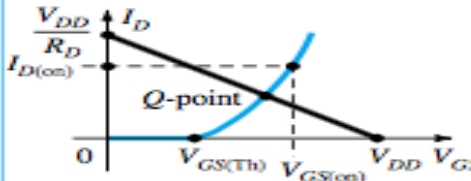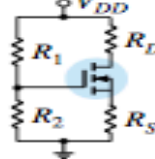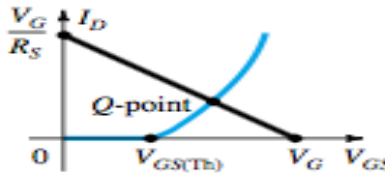Depletion-type MOSFET Fixed-bias		$V_{GSQ} = +V_{GG}$ $V_{DS} = V_{DD} - I_D R_D$	
Depletion-type MOSFET Voltage-divider bias		$V_G = \frac{R_2 V_{DD}}{R_1 + R_2}$ $V_{GS} = V_G - I_S R_S$ $V_{DS} = V_{DD} - I_D (R_D + R_S)$	
Enhancement type MOSFET Feedback configuration		$V_{GS} = V_{DS}$ $V_{GS} = V_{DD} - I_D R_D$	
Enhancement-type MOSFET Voltage-divider bias		$V_G = \frac{R_2 V_{DD}}{R_1 + R_2}$ $V_{GS} = V_G - I_D R_S$	

Break



FET Transistors

AC Analysis:

FETs provide:

- Excellent voltage gain
- High input impedance
- Low-power consumption
- Good frequency response



FET Transistors

AC Analysis:

Transconductance: The ratio of a change in I_D to the corresponding change in V_{GS}

- Transconductance is denoted g_m and given by:

$$g_m = \frac{\Delta I_D}{\Delta V_{GS}}$$



FET Transistors

Mathematical Definitions of g_m

$$g_m = \frac{2I_{DSS}}{|V_P|} \left[1 - \frac{V_{GS}}{V_P} \right]$$

For $V_{GS} = 0 \text{ V}$


$$g_{m0} = \frac{2I_{DSS}}{|V_P|}$$

$$g_m = g_{m0} \left[1 - \frac{V_{GS}}{V_P} \right] = g_{m0} \sqrt{\frac{I_D}{I_{DSS}}}$$



FET Transistors



FET AC Equivalent Circuit

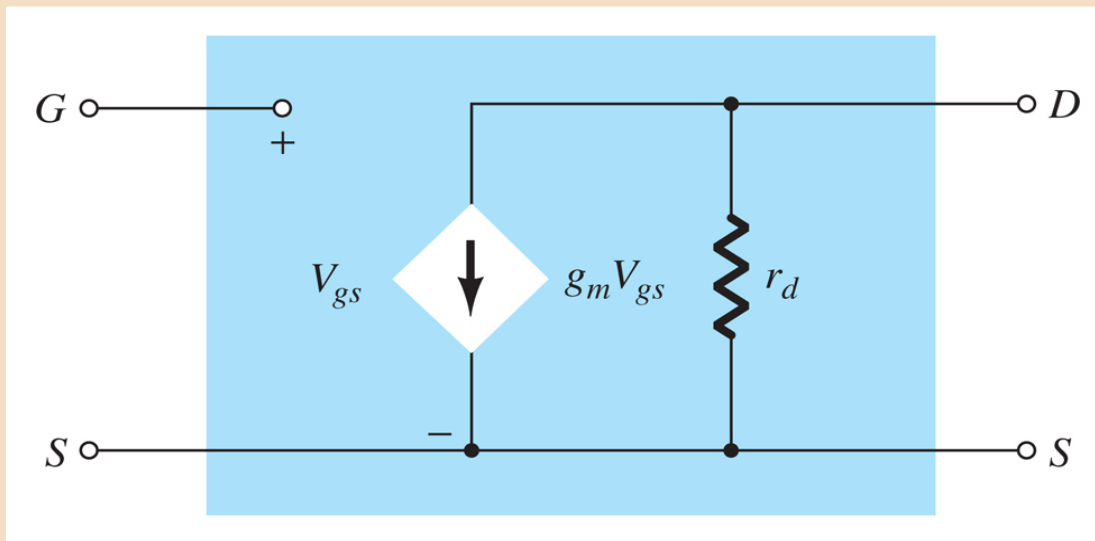




FET Transistors

Common-Source (CS) Fixed-Bias

  

FET Transistors

Common-Source (CS) Fixed-Bias

 

Input impedance:

$$Z_i = R_G$$

$$Z_o = R_D || r_d$$

$$Z_o \cong R_D \Big|_{r_d \geq 10 R_D}$$



$$A_v = \frac{V_o}{V_i} = -g_m (r_d || R_D)$$

$$A_v = \frac{V_o}{V_i} = -g_m R_D \Big|_{r_d \geq 10 R_D}$$



FET Transistors

AC Analysis (self bias)

 
 




EEC2146: Electronic Circuits and Measurements

FET Transistors

AC Analysis (self bias)

  

$$Z_i = R_G$$

$$Z_o = r_d || R_D$$

$$Z_o \cong R_D \Big|_{r_d \geq 10 R_D}$$

$$A_v = -g_m (r_d || R_D)$$


$$A_v = -g_m R_D \Big|_{r_d \geq 10 R_D}$$



EEC2146: Electronic Circuits and Measurements

FET Transistors

AC Analysis (self bias)

 

$$Z_i = R_G$$

$$Z_o \cong R_D \quad \left| \quad r_d \geq 10 R_D \right.$$



$$A_v = \frac{V_o}{V_i} = - \frac{g_m R_D}{1 + g_m R_S + \frac{R_D + R_S}{r_d}}$$

$$A_v = \frac{V_o}{V_i} = - \frac{g_m R_D}{1 + g_m R_S} \quad \left| \quad r_d \geq 10 (R_D + R_S) \right.$$



FET Transistors

AC Analysis (voltage divider)

  




EEC2146: Electronic Circuits and Measurements

FET Transistors

AC Analysis (voltage divider)

 

$$Z_i = R_1 \parallel R_2$$

$$Z_o = r_d \parallel R_D$$

$$Z_o \cong R_D \quad \left| \quad r_d \geq 10 R_D \right.$$



$$A_v = -g_m (r_d \parallel R_D)$$

$$A_v = -g_m R_D \quad \left| \quad r_d \geq 10 R_D \right.$$



FET Transistors

Source Follower (Common-Drain)

  




FET Transistors

Source Follower (Common-Drain)

$$Z_i = R_G$$

 

$$Z_o = r_d \parallel R_S \parallel \frac{1}{g_m}$$



$$Z_o \cong R_S \parallel \frac{1}{g_m} \Big|_{r_d \geq 10 R_S}$$

$$A_v = \frac{V_o}{V_i} = \frac{g_m (r_d \parallel R_S)}{1 + g_m (r_d \parallel R_S)}$$

$$A_v = \frac{V_o}{V_i} = \frac{g_m R_S}{1 + g_m R_S} \Big|_{r_d \geq 10}$$

FET Transistors

Common-Gate (CG) Circuit

  




EEC2146: Electronic Circuits and Measurements

FET Transistors

Common-Gate (CG) Circuit

 

$$Z_i = R_S \parallel \left[\frac{r_d + R_D}{1 + g_m r_d} \right]$$

$$Z_i \cong R_S \parallel \frac{1}{g_m} \Big|_{r_d \geq 10 R_D}$$

$$Z_o = R_D \parallel r_d$$

$$Z_o \cong R_D \Big|_{r_d \geq 10}$$

$$A_v = \frac{V_o}{V_i} = \frac{\left[g_m R_D + \frac{R_D}{r_d} \right]}{\left[1 + \frac{R_D}{r_d} \right]}$$

$$A_v = g_m R_D \Big|_{r_d \geq 10 R_D}$$




EEC2146: Electronic Circuits and Measurements



FET Transistors

D-Type MOSFET AC Equivalent


 




FET Transistors

Enhancement -Type MOSFET AC Equivalent



$$g_m = 2k(V_{GS_Q} - V_{GS(Th)})$$

  



FET Transistors

Common-Source Drain-Feedback

  




EEC2146: Electronic Circuits and Measurements

FET Transistors

Common-Source Drain-Feedback

 

$$Z_i = \frac{R_F + r_d \parallel R_D}{1 + g_m(r_d \parallel R_D)}$$

$$Z_i \cong \frac{R_F}{1 + g_m R_D} \Big|_{R_F \gg r_d \parallel R_D, r_d \geq 10 R_D}$$

$$Z_o = R_F \parallel r_d \parallel R_D$$



$$Z_o \cong R_D \Big|_{R_F \gg r_d \parallel R_D, r_d \geq 10 R_D}$$

$$A_v = -g_m(R_F \parallel r_d \parallel R_D) \quad A_v \cong -g_m R_D \Big|_{R_F \gg r_d \parallel R_D, r_d \geq 10 R_D}$$



FET Transistors


Common-Source Voltage-Divider Bias

  



FET Transistors

Common-Source Voltage-Divider Bias

 

$$Z_i = R_1 \parallel R_2$$

$$Z_o = r_d \parallel R_D$$

$$Z_o \cong R_D \big|_{r_d \geq 10 R_D}$$

$$A_v = -g_m (r_d \parallel R_D) \quad A_v \cong -g_m R_D \big|_{r_d \geq 10 R_D}$$



EEC2146: Electronic Circuits and Measurements



Questions